

Lab 2. ModelSim VHDL 1 of 4 Decoder

1 of 4 Decoder with active low outputs. See the truth table below, but don't create the gates directly, instead **use two (nested) IF statements** to design the decoder. Decoder enable (i_EN) is active low. If i_EN is high, then all 4 outputs are high, i.e., turned off, because the Y outputs are active low). You should use std_logic for the i_EN pin and for select pins i_B and i_A (pin i_B is the MSB). Use a 2-bit std_logic_vector for internal signal w_BA consisting of i_B & i_A (concatenated). Use a 4 bit std_logic_vector o_Y for your output pins. Write a testbench that tests all 4 combinations of the w_BA select lines with i_EN low (enabled), then test all 4 combinations of the select lines with i_EN high (disabled).

DECODERS

Another common MSI circuit is the *decoder* (also called a *demultiplexer*). A decoder is an arrangement of gates that allows a single enable or data input to be sent to several destinations. A decoder circuit along with its MSI symbol is shown in Fig. 3-18. This is a two-line to four-line decoder (also called a one out of four). Two select inputs A and B determine which of four outputs Y_0 through Y_3 will be connected to the enable or data input.

Enable	B	A	Y_3	Y_2	Y_1	Y_0
1	X	X	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

 


Figure 3-18 Decoder.

- For credit for this assignment, use the NANDland naming style and the coding style in my powerpoints: Submit:
 - Your decoder.vhd and decoder_tb files.
 - The ModelSim waveform from the testbench.
(You can save an image of the waveform using Windows to SNIP a screenshot of the image).

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity decoder is
    port (
        i_EN : in std_logic;
        i_A  : in std_logic;
        i_B  : in std_logic;

        o_Y : out std_logic_vector(3 downto 0)
    );
end decoder;

architecture Behavioral of decoder is
    Signal w_BA : std_logic_vector(1 downto 0);
begin
    w_BA <= i_B & i_A;
    process(w_BA, i_EN)
    begin
        if i_EN = '1' then o_Y <= "1111";
        else
            if w_BA = "00" then o_Y <= "1110";
            elsif w_BA = "01" then o_Y <= "1101";
            elsif w_BA = "10" then o_Y <= "1011";
            elsif w_BA = "11" then o_Y <= "0111";
            end if;
        end if;
    end process;
end Behavioral;

```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity tb_decoder is
end entity tb_decoder;
```

architecture behaviour of tb_decoder is

```
-- Use Unit Under Test (UUT)
component decoder
port (
    i_EN : in std_logic;
    i_A  : in std_logic;
    i_B  : in std_logic;
    o_Y  : out std_logic_vector(3 downto 0)
);
end component;

-- Signals for input and output
signal test_i_EN : std_logic := '0';
signal test_i_A  : std_logic := '0';
signal test_i_B  : std_logic := '0';
signal test_o_Y  : std_logic_vector(3 downto 0);
```

begin

```
-- Instantiate the decoder
uut: decoder
port map (
    i_EN => test_i_EN,
    i_A  => test_i_A,
    i_B  => test_i_B,
    o_Y  => test_o_Y
);

-- Stimulus process
process
begin
    -- Test with Enable = 1 (Output should be "1111" regardless of inputs)
    test_i_EN <= '1';
    test_i_A  <= '0';
    test_i_B  <= '0';
    wait for 50 ns;

    test_i_A <= '1';
    wait for 50 ns;
```

```
test_i_B <= '1';
wait for 50 ns;

test_i_A <= '0';
wait for 50 ns;

-- Test with Enable = 0 (Decoder active)
test_i_EN <= '0';

-- Apply all 4 combinations of i_A and i_B
test_i_A <= '0';
test_i_B <= '0';
wait for 50 ns;

test_i_A <= '0';
test_i_B <= '1';
wait for 50 ns;

test_i_A <= '1';
test_i_B <= '0';
wait for 50 ns;

test_i_A <= '1';
test_i_B <= '1';
wait for 50 ns;

-- End simulation
assert false
report "End of simulation."
severity failure;
end process;
end behaviour;
```